

## Analog – Problem 1.1.56

ee25btech11056 – Suraj.N

March 24, 2026

# Problem Statement

## Problem 1.1.56

Consider the triangular wave generator shown in Fig. 1.1.56.1. Assume ideal op-amps with  $\pm 2\text{ V}$  supply. The input is a  $+5\text{ V}$ ,  $50\text{ Hz}$  square wave with  $50\%$  duty cycle.

The condition that results in a triangular wave of  $5\text{ V}$  peak-to-peak and  $50\text{ Hz}$  at the output is:

- ①  $RC = 1$
- ②  $R/C = 1$
- ③  $R/C = 5$
- ④  $C/R = 5$

# Circuit Diagram

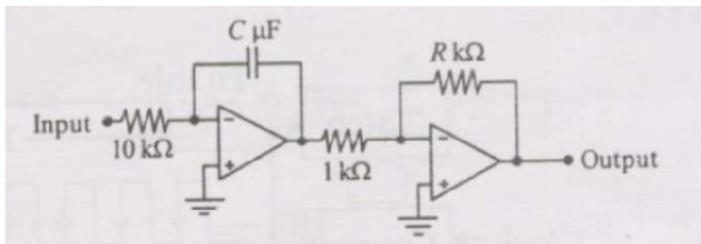


Fig : Circuit

## Step 1: Deriving Output of Integrator Circuit

For an ideal op-amp with negative feedback:

- 1 The open-loop gain  $A \rightarrow \infty$
- 2 The differential input voltage  $V^+ - V^- \rightarrow 0$
- 3 Since  $V^+ = 0$  (grounded), we get  $V^- = 0$

The inverting terminal is therefore at **virtual ground**:

$$V^- = V^+ = 0 \text{ V}$$

This means the voltage across  $R_1$  is simply  $V_{\text{in}} - 0 = V_{\text{in}}$ .

The current through  $R_1$  flowing into the virtual ground node is:

$$i_{R_1}(t) = \frac{V_{\text{in}}(t) - V^-}{R_1} = \frac{V_{\text{in}}(t)}{R_1}$$

## Step 2: KCL at the Inverting Terminal

Since the ideal op-amp draws **zero input current**, all of  $i_{R_1}$  must flow through the capacitor  $C$ .

Applying KCL at the inverting node  $V^-$ :

$$i_C(t) = \frac{V_{\text{in}}(t)}{R_1}$$

The voltage-current relationship for the capacitor is:

$$i_C(t) = C \frac{d}{dt}(V^- - V_{\text{out}}(t)) = C \frac{d}{dt}(0 - V_{\text{out}}(t)) = -C \frac{dV_{\text{out}}(t)}{dt}$$

## Step 3: Differential Equation

Equating the two expressions for  $i_C(t)$ :

$$-C \frac{dV_{\text{out}}(t)}{dt} = \frac{V_{\text{in}}(t)}{R_1}$$

Rearranging:

$$\frac{dV_{\text{out}}(t)}{dt} = -\frac{V_{\text{in}}(t)}{R_1 C}$$

This is the governing differential equation of the inverting integrator. The output voltage changes at a rate proportional to the input voltage, with a sign inversion and scaling by  $\frac{1}{R_1 C}$ .

## Step 4: Integration to Get Output Formula

Integrating both sides of the differential equation from 0 to  $t$ :

$$\int_0^t \frac{dV_{\text{out}}(\tau)}{d\tau} d\tau = -\frac{1}{R_1 C} \int_0^t V_{\text{in}}(\tau) d\tau$$

The left side evaluates directly:

$$V_{\text{out}}(t) - V_{\text{out}}(0) = -\frac{1}{R_1 C} \int_0^t V_{\text{in}}(\tau) d\tau$$

Assuming the capacitor is initially uncharged,  $V_{\text{out}}(0) = 0$ :

$$V_{\text{out}}(t) = -\frac{1}{R_1 C} \int_0^t V_{\text{in}}(\tau) d\tau$$

This is the **inverting integrator output formula**.

## Circuit Description

The circuit has two stages:

- 1 **Stage 1 – Inverting Integrator:** input resistor  $R_1 = 10 \text{ k}\Omega$ , feedback capacitor  $C \mu\text{F}$ . Converts the square wave to a triangular ramp.
- 2 **Stage 2 – Inverting Amplifier:** input resistor  $1 \text{ k}\Omega$ , feedback resistor  $R \text{ k}\Omega$ . Inverts and scales the triangular ramp.

The transfer functions are:

$$V_{\text{int}}(t) = -\frac{1}{R_1 C} \int_0^t V_{\text{in}}(\tau) d\tau$$

$$V_{\text{out}} = -\frac{R [\text{k}\Omega]}{1 [\text{k}\Omega]} V_{\text{int}} = -R V_{\text{int}}$$



## Input Signal

The input is a bipolar square wave of amplitude  $V_p = 5\text{ V}$ :

$$V_{\text{in}}(t) = \begin{cases} +5\text{ V} & 0 \leq t < T/2 \\ -5\text{ V} & T/2 \leq t < T \end{cases}$$

The time parameters are:

- ❶ Frequency:  $f = 50\text{ Hz}$
- ❷ Period:  $T = 1/f = 20\text{ ms}$
- ❸ Half-period:  $T/2 = 10\text{ ms} = 0.01\text{ s}$
- ❹ Amplitude:  $V_p = 5\text{ V}$

A bipolar square wave integrated over each half-period produces a linear ramp. Alternating positive and negative half-cycles produce a triangular wave at Stage 1 output.

## Stage 1: Integrator Analysis

The ramp magnitude over one half-period is:

$$\Delta V_{\text{int}} = \frac{V_p \cdot (T/2)}{R_1 \cdot C}$$

Substituting  $V_p = 5 \text{ V}$ ,  $T/2 = 0.01 \text{ s}$ ,  $R_1 = 10^4 \Omega$ ,  $C_1 = C \times 10^{-6} \text{ F}$ :

$$\Delta V_{\text{int}} = \frac{5 \times 0.01}{10^4 \times C \times 10^{-6}} = \frac{0.05}{0.01 C} = \frac{5}{C} \text{ V}$$

Since the  $-5 \text{ V}$  half-cycle produces an equal upward ramp, the peak-to-peak at Stage 1 output is:

$$\Delta V_{\text{int,pp}} = \frac{5}{C} \text{ V}$$

## Stage 2: Amplifier

Stage 2 gain magnitude:

$$|A_v| = \frac{R [\text{k}\Omega]}{1 [\text{k}\Omega]} = R$$

Peak-to-peak at Stage 2 output:

$$V_{\text{out,pp}} = R \times \frac{5}{C} = \frac{5R}{C}$$

Setting  $V_{\text{out,pp}} = 5 \text{ V}$ :

$$\frac{5R}{C} = 5 \quad \implies \quad \frac{R}{C} = 1$$

# Plot of Waveforms

## Problem 1.1.56 — Triangular Wave Generator

$$R_1 = 10\text{ k}\Omega, R = 1\text{ k}\Omega, C = 1\text{ }\mu\text{F}, R/C = 1$$

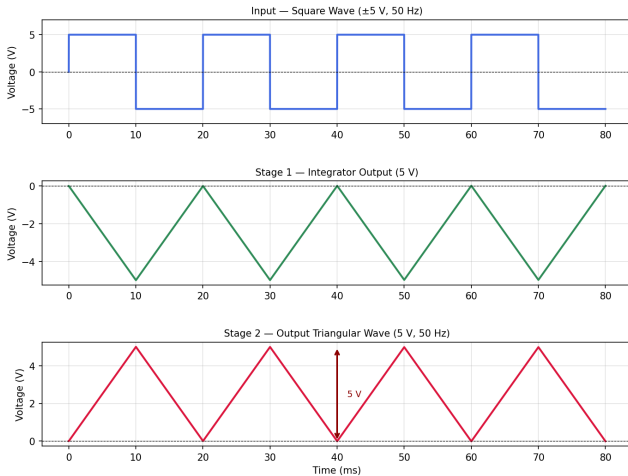


Fig : Waveforms

# Python Code: Verification

```
import numpy as np

# Given
Vin_amp = 5.0 # Bipolar square wave amplitude (V), i.e. 5 V
f = 50 # Hz
T = 1.0 / f # Period = 20 ms
R1 = 10**4 # Integrator input resistor = 10 k ( )
R_in2 = 10**3 # Stage-2 input resistor = 1 k ( )

# Analysis
# During the +5V half-cycle, integrator ramps DOWN by delta.
# During the 5V half-cycle, integrator ramps UP by delta.
# Net peak-to-peak at Stage-1 output = delta (one half-swing).

r_c = (5*2*R1)/(Vin_amp*T)

r_c = r_c / 10**6

print(f"The value of R/C = {r_c}")
```

# Python Code: Waveform Simulation

```
"""
plot_waveforms_1156.py Problem 1.1.56
Simulate and plot waveforms for the triangular wave generator.
Condition:  $RC = 1$  ( $R = 1\text{ k}$ ,  $C = 1\text{ F}$ )
"""

import numpy as np
import matplotlib.pyplot as plt
import matplotlib.gridspec as gridspec

# Parameters
Vin_amp = 5.0 # Bipolar square wave amplitude (V)
f = 50 # Hz
T = 1 / f # Period = 20 ms
R1 = 10e3 # Integrator input resistor () = 10 k
C = 1e-6 # Capacitor (F) = 1 F
R2 = 1e3 # Stage-2 feedback resistor () = 1 k
R_in2 = 1e3 # Stage-2 input resistor () = 1 k
gain2 = R2 / R_in2 # = 1

dt = T / 2000
t = np.arange(0, 4 * T, dt)

# Input: bipolar square wave 5 V
Vin = Vin_amp * np.sign(np.sin(2 * np.pi * f * t))

# Stage 1: Inverting integrator (Euler)
Vint = np.zeros(len(t))
for i in range(1, len(t)):
    Vint[i] = Vint[i - 1] - (Vin[i - 1] / (R1 * C)) * dt
```

# Python Code: Waveform Simulation

```
# Stage 2: Inverting amplifier
Vout = -gain2 * Vint

# Measure pp after settling
mask = t > T
Vpp_out = Vout[mask].max() - Vout[mask].min()
Vpp_int = Vint[mask].max() - Vint[mask].min()

# Plot
fig = plt.figure(figsize=(11, 8))
fig.suptitle(
    "Problem 1.1.56 Triangular Wave Generator\n"
    r"$R_1 = 10\,\mathrm{k}\Omega$, \;\; $R_2 = 1\,\mathrm{k}\Omega$, \;\; $"
    r"$C_1 = 1\,\mu\mathrm{F}$, \;\; $R/C_1 = 1$",
    fontsize=13, fontweight='bold'
)
gs = gridspec.GridSpec(3, 1, hspace=0.55)
t_ms = t * 1e3

# Panel 1: Input
ax1 = fig.add_subplot(gs[0])
ax1.plot(t_ms, Vin, color='royalblue', lw=2.0)
ax1.set_title('Input Square Wave (5 V, 50 Hz)', fontsize=10)
ax1.set_ylabel('Voltage (V)')
ax1.set_ylim(-7, 7)
ax1.axhline(0, color='k', lw=0.6, ls='--')
ax1.grid(True, alpha=0.35)
```

# Python Code: Waveform Simulation

```
# Panel 2: Integrator output
ax2 = fig.add_subplot(gs[1])
ax2.plot(t_ms, Vint, color='seagreen', lw=2.0)
ax2.set_title(
    f'Stage_1_Integrator_Output_(5_V)',
    fontsize=10
)
ax2.set_ylabel('Voltage_(V)')
ax2.axhline(0, color='k', lw=0.6, ls='--')
ax2.grid(True, alpha=0.35)

# Panel 3: Final output
ax3 = fig.add_subplot(gs[2])
ax3.plot(t_ms, Vout, color='crimson', lw=2.0)
ax3.set_title(
    f'Stage_2_Output_Triangular_Wave_(5_V, 50_Hz)',
    fontsize=10
)
ax3.set_ylabel('Voltage_(V)')
ax3.set_xlabel('Time_(ms)')
ax3.axhline(0, color='k', lw=0.6, ls='--')
ax3.grid(True, alpha=0.35)
# Annotate peak-to-peak arrow
y_max = Vout[mask].max()
y_min = Vout[mask].min()
x_ann = t_ms[mask][len(t_ms[mask])//3]
ax3.annotate('', xy=(x_ann, y_min), xytext=(x_ann, y_max), arrowprops=dict(arrowstyle='<->', color='darkred',
    lw=1.8))
ax3.text(x_ann + 1.5, (y_max + y_min) / 2, f'5_V', color='darkred', fontsize=9, va='center')
plt.savefig('waveforms.png', dpi=150, bbox_inches='tight')
plt.show()
```